
 


Design with Tri-State Buffers

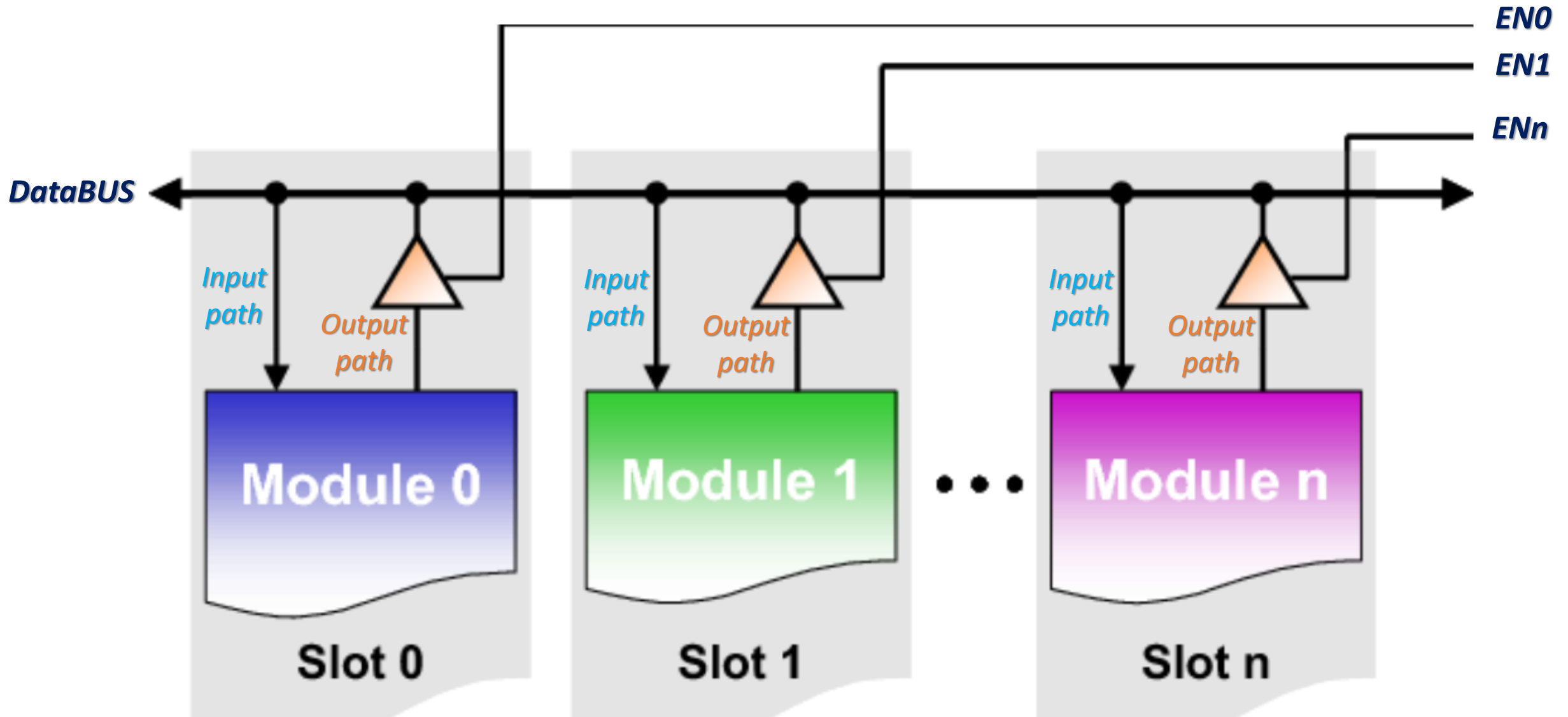

Bi-directional BUS



inout Pin synthesis - Bidirectional Pin


```
entity BidirPinBasic is
    port(
        writePin: in    std_logic;
        readPin:  out   std_logic;
        bidirPin: inout std_logic
    );
end BidirPin;

architecture comb of BidirPinBasic is
begin


    readPin <= bidirPin;
    bidirPin <= writePin;

end comb;
```

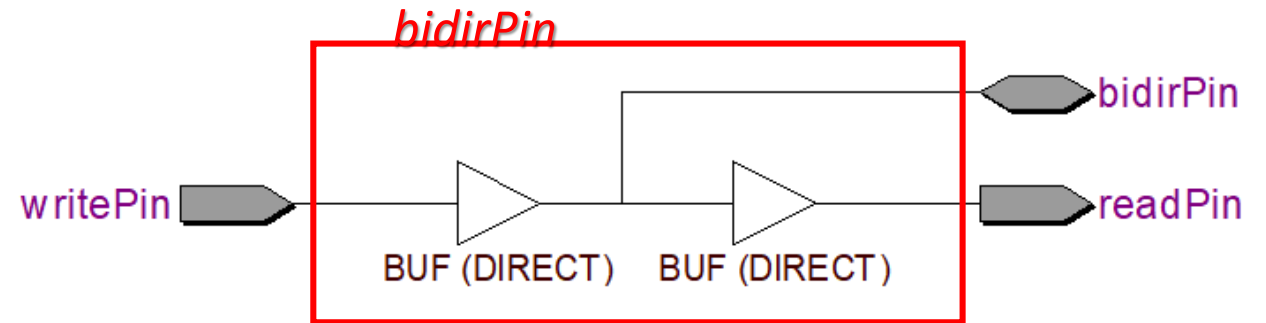*Reading and writing from **inout** module pin is synthesized via buffer (as shown in the above RTL synthesis)*



Cyclone II I/O Features

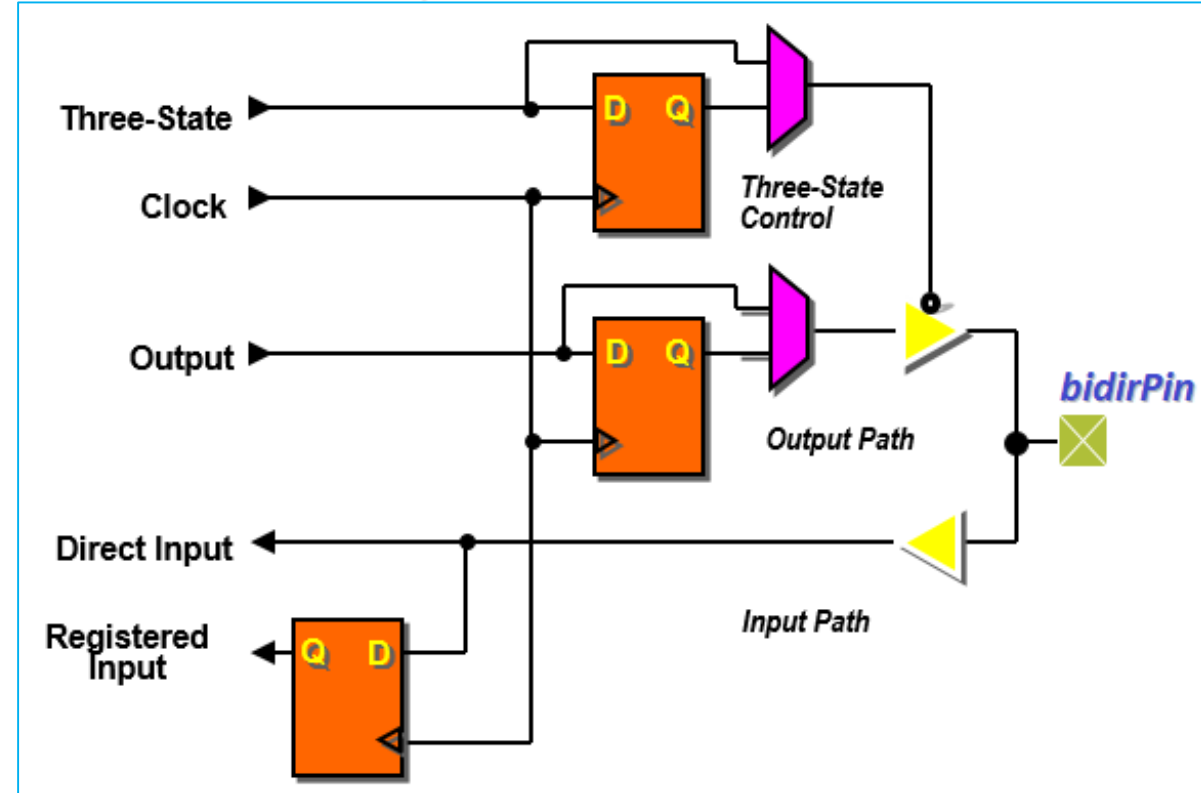


Bi-directional BUS

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity BidirPin is
5      generic( width: integer:=16 );
6      port(
7          Dout: in      std_logic_vector(width-1 downto 0);
8          en:   in      std_logic;
9          Din:  out     std_logic_vector(width-1 downto 0);
10         IOpin: inout  std_logic_vector(width-1 downto 0)
11     );
12 end BidirPin;
13
14 architecture comb of BidirPin is
15 begin
16     Din <= IOpin;
17     IOpin <= Dout when(en='1') else (others => 'Z');
18
19 end comb;

```

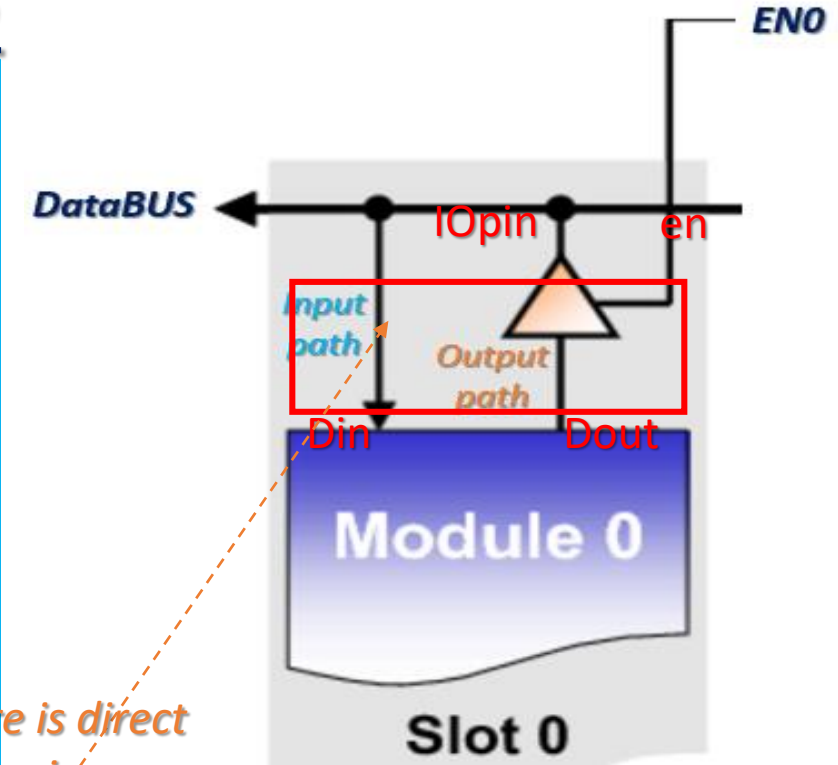

There is direct galvanic connection but via buffer

